



**RV College of Engineering®**

Mysore Road, RV Vidyaniketan Post,  
Bengaluru - 560059, Karnataka, India

# **LICA Open ended experiment report**

Aahana Nischal

1RV23ET001

## **Simulation of astable multivibrator using MATLAB**



# Contents

1. Aim
2. Working
3. Circuit diagram
4. Equations
5. MATLAB Code
6. Simulation results

## Aim

To simulate an astable multivibrator using MATLAB and analyze its behavior by observing the output waveforms. The simulation will demonstrate the generation of a continuous square wave signal through the oscillations of the circuit.

## Working


The astable multivibrator works as a square wave generator. The output of the opamp is fed back to its non-inverting terminal - Resistors  $R_1$  and  $R_2$  form a feedback network and a fraction of the output ( $\beta = R_2 / (R_1 + R_2)$ ) is fed back as the input.

The capacitor  $C$  charges to  $+V_{sat}$  through resistor  $R$ . The voltage at the non inverting terminal of the opamp is held at  $+\beta V_{sat}$  as indicated by the use of the  $R_1$ - $R_2$  potential divider network.

The charging continues until the voltage at the negative terminal of the opamp is just greater than the voltage at the non-inverting terminal ( $+\beta V_{sat}$ ). When this happens the output voltage switches down to  $-V_{sat}$ .

The voltage at the inverting terminal becomes more negative and at one point exceeds  $-\beta V_{sat}$  and then the output switches back to  $+V_{sat}$ . This cycle repeats.

## Circuit Diagram

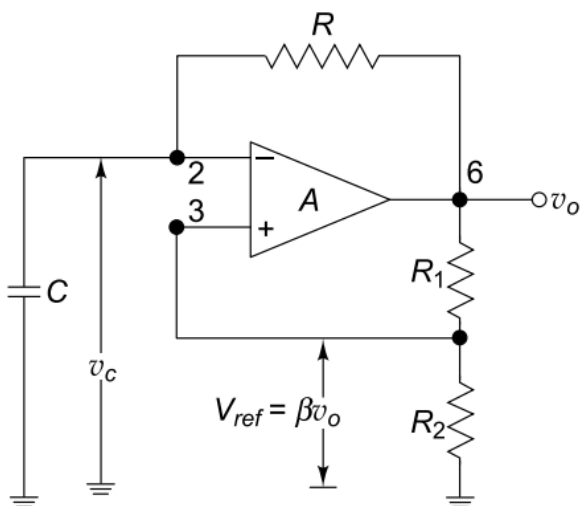

## Equations

$$v_c(t) = +V_{sat} + (-\beta V_{sat} - V_{sat}) e^{\frac{-t}{RC}}$$

$$\beta V_{sat} = V_{sat} \left( 1 - (1 + \beta) e^{\frac{-T_1}{RC}} \right)$$

$$(1 - \beta) = (1 + \beta) e^{\frac{-T_1}{RC}}$$

$$T_1 = RC \ln \frac{1 + \beta}{1 - \beta} = RC \ln \frac{R_1 + 2R_2}{R_1}$$

$$T = 2T_1 = 2RC \ln \frac{1 + \beta}{1 - \beta}$$

$$T = 2 RC \ln \left( \frac{R_1 + 2R_2}{R_1} \right)$$

$$f_o = \frac{1}{T} = \frac{1}{2 RC \ln \left( \frac{1 + \beta}{1 - \beta} \right)}$$

$$f_o = \frac{1}{2RC \ln 3} = \frac{1}{2.2RC}$$



## MATLAB Code

```
% Parameters for the astable multivibrator circuit
R1 = 483.2e3;      % Resistor 1 value (Ohms)
R2 = 483.2e3;      % Resistor 2 value (Ohms)
C = 1e-6;          % Capacitor value (Farads)
Vcc = 5;           % Supply voltage (Volts)
Vth_low = 1.5;     % Lower threshold voltage (Volts)
Vth_high = 3.5;    % Upper threshold voltage (Volts)

% Time settings
Tmax = 5;          % Maximum time to simulate (seconds)
dt = 1e-5;         % Time step (seconds)
t = 0:dt:Tmax;     % Time vector

% Initial conditions
V_C = 0;           % Initial capacitor voltage (Volts)
output = zeros(size(t)); % Output square waveform
charge = true;      % Flag for charging the capacitor

% Store capacitor voltage for plotting
V_C_values = zeros(size(t));

% Simulation of charging and discharging behavior
for i = 2:length(t)
    % Charging phase
    if charge
        V_C = V_C + (Vcc - V_C) / (R1 * C) * dt; % Exponential charge
        if V_C >= Vth_high % Switch to discharge when voltage reaches upper threshold
            charge = false;
            output(i) = 0; % Output goes low during discharge
        else
            output(i) = 1; % Output goes high during charge
        end
    % Discharging phase
    else
        V_C = V_C - V_C / (R2 * C) * dt; % Exponential discharge
        if V_C <= Vth_low % Switch to charge when voltage reaches lower threshold
            charge = true;
            output(i) = 1; % Output goes high during charge
        else
            output(i) = 0; % Output stays low during discharge
        end
    end
    % Store the capacitor voltage for plotting
    V_C_values(i) = V_C;
end

% Adjust both the capacitor voltage and output to oscillate from -5V to +5V
V_C_values_adjusted = V_C_values - 2.5; % Shift capacitor voltage to oscillate around 0V
output_adjusted = (output - 0.5) * Vcc; % Shift output to oscillate between -2.5V and +2.5V

% Plot capacitor voltage and output square waveform in the same plot
figure;
plot(t, V_C_values_adjusted, 'LineWidth', 1.5, 'DisplayName', 'Capacitor Voltage');
hold on;
plot(t, output_adjusted, 'LineWidth', 1.5, 'DisplayName', 'Output Square Wave'); % Output wave scaled
xlabel('Time (seconds)');
ylabel('Voltage (V)');
title('Capacitor Voltage and Output Square Waveform');
legend('show');
grid on;

% Set y-axis limits from -5V to +5V
ylim([-5, 5]);
```



## Simulation Results

